

A Discrete Successive-Approximation-ADC

Implemented to learn about/demonstrate the workings of this ADC Architecture, not to design an effective ADC.

Sheets/Breakdown:

PWR:
Power Input & Voltage Regulation

Input:
Analog Voltage Input to the ADC

Clock:
NE555-based clock used to drive state machine. Adjustable in Frequency from approx. 1Hz to 170Hz

State Machine:
The State machine that sequences the conversion.

SA-Register:
The Successive-Approximation (SA) Register used during conversion.

Analog:
The Analog-domain section of the ADC. This includes the comparator and the DAC: An R2R DAC fed by the output of the SA-Register and the state machine. This output is buffered to remove switching noise.

Output:
The output register into which the result is latched once a conversion finishes. Also contains a simple binary Display of the final conversion result.

Philipp Schilk

Sheet: /
File: SA-ADC.sch


Title: Schilk_SA-ADC

Size: A4 Date: 2020-06-11

KiCad E.D.A. kicad (5.1.5)-3

Rev: v0.1

Id: 1/9

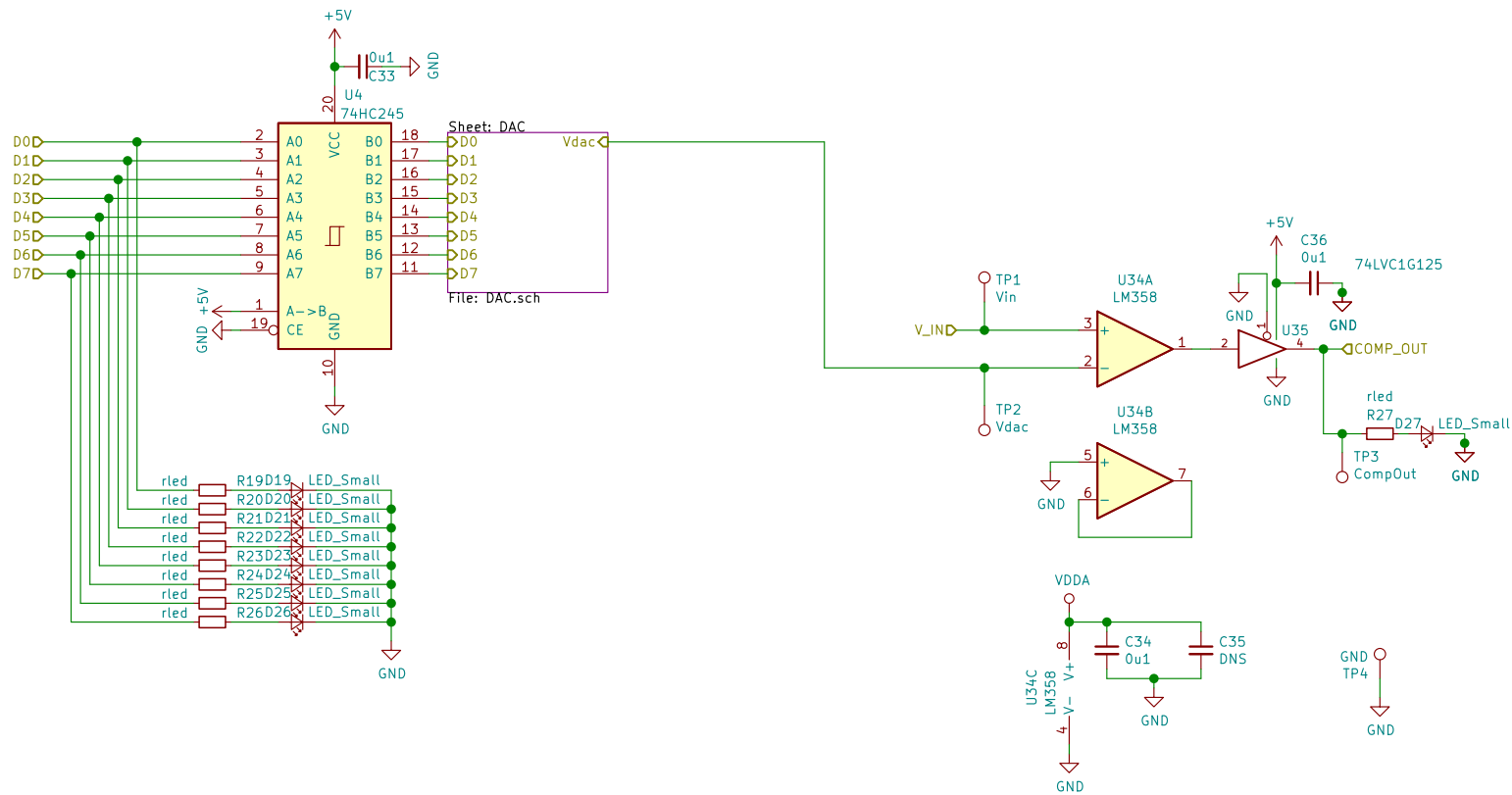

Sheet: /Analog/
File: Analog.sch


Title: Schilk_SA-ADC

Size: A4 Date: 2020-02-03

KiCad E.D.A. kicad (5.1.5)-3

Rev: v0.0 (Prod.)

Id: 2/9

 

R2R DAC
Use Precision Resistors, Optimally <0.5%

Sheet: /Analog/DAC/
File: DAC.sch

Title: Schilk_SA-ADC


Size: A4 Date: 2020-02-03

KiCad E.D.A. kicad (5.1.5)-3

Rev: v0.0 (Prod.)

Id: 3/9

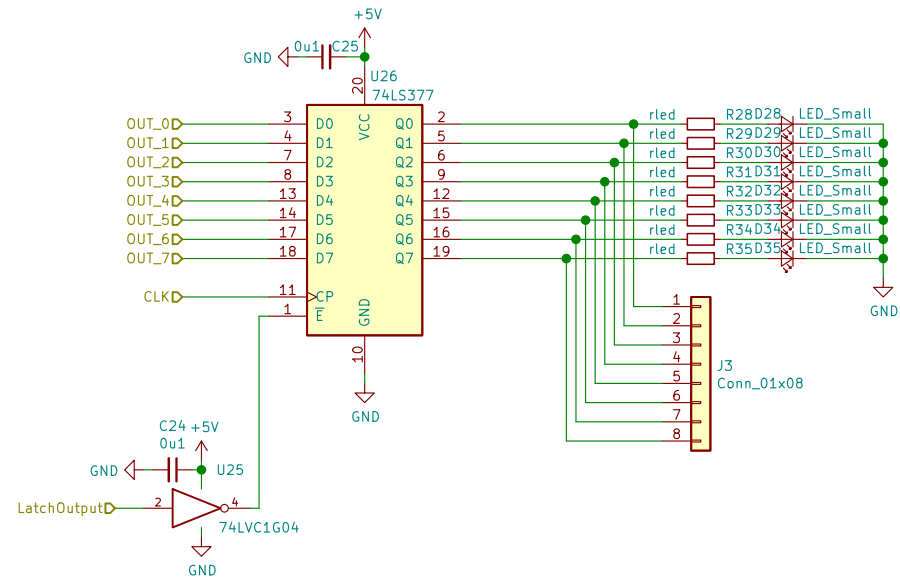Results are latched into this register to make space
in the SA Register for the next conversion.



Sheet: /Output/
File: Output.sch


Title: Schilk_SA-ADC

Size: A4
KiCad E.D.A. kicad (5.1.5)-3

Date: 2020-02-03

Rev: v0.0 (Prod.)





Id: 4/9

 

H1
MountingHole

H2
MountingHole

Sheet: /PWR/		
File: PWR.sch		
Title: Schilk_SA-ADC		
Size: A4	Date: 2020-02-03	Rev: v0.0 (Prod.)
KiCad E.D.A. kicad (5.1.5)-3		Id: 5/9

 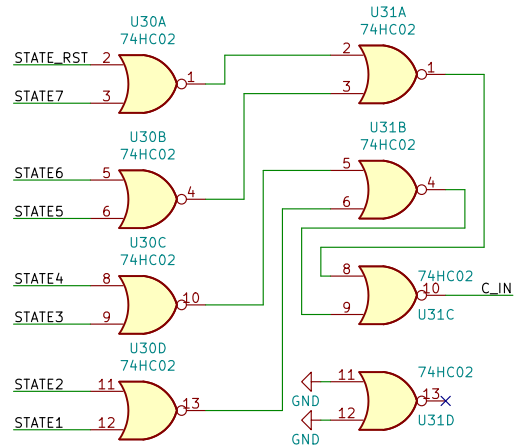 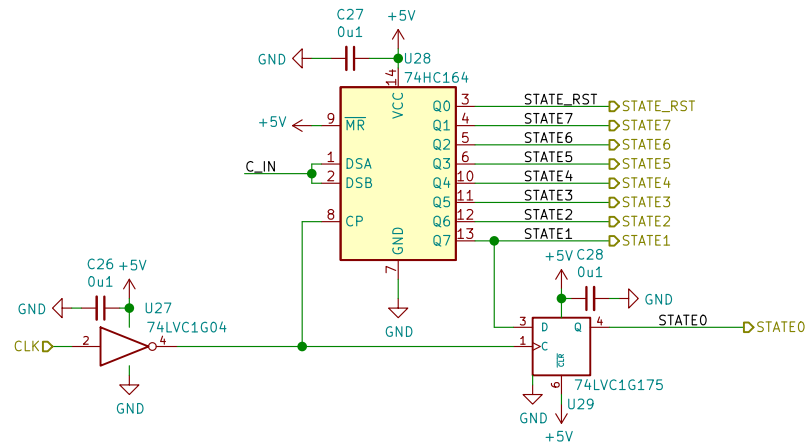

Generates the Sequential Signals that decide the state of the converter.

D-FlipFlop U29 essentially provides a 9th stage to the shift register U28

NOR Gates U30 and U31 enable the shift-in signal of the register once the first 8 stages are empty.

During operation it would be sufficient to tie STATE0 to the shift-in, but this circuit ensures proper operation of the state machine after at most 1 cycle through all states, no matter what the initial value of the register after power up is.

This shift register operates on the falling edge of the clock. This avoids race conditions:

All signals are set up by the state machine on the falling clock edge, and are latched into the registers on the rising clock.

Sheet: /StateMaschine.sch/
File: StateMaschine.sch


Title: Schilk_SA-ADC

Size: A4 Date: 2020-02-03

KiCad E.D.A. kicad (5.1.5)-3

Rev: v0.0 (Prod.)

Id: 7/9

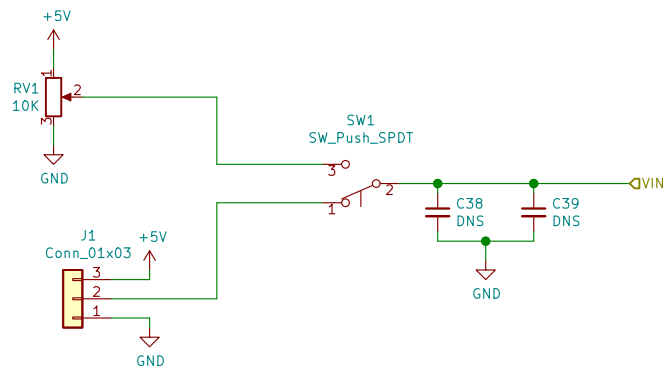

SW1 Allows selection between the internal potentiometer or an external voltage input to be fed to the ADC.

Sheet: /Input/
File: Input.sch

Title: Schilk_SA-ADC

Size: A4 Date: 2020-02-03

KiCad E.D.A. kicad (5.1.5)-3

Rev: v0.0 (Prod.)

Id: 8/9

